

Valeur moyenne et Valeur efficace
d'un signal à la sortie d'un
redresseur


القيمة المتوسطة والقيمة الفعالة
 عند مخرج مقوم

رياضياً تعرف بـ = المقادير كما يلي :

القيمة المتوسطة $V_{moy} = \frac{1}{T} \int_0^T V(t) dt$

القيمة الفعالة $V_{eff} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$

1) Redresseur simple alternatif :

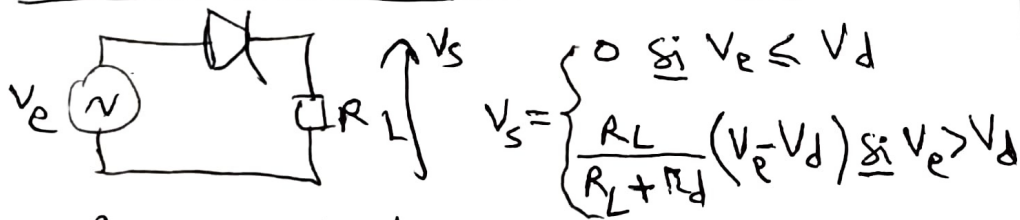

$$v_s = \begin{cases} 0 & \text{si } v_e \leq V_d \\ \frac{R_L}{R_L + R_d} (v_e - V_d) & \text{si } v_e > V_d \end{cases}$$

* Pour une diode idéale : $V_d = 0$ et $R_d = 0$

$$\Rightarrow v_s = \begin{cases} 0 & \text{si } v_e \leq 0 \\ v_e & \text{si } v_e > 0 \end{cases}$$

a) Valeur moyenne :

$$V_s(moy) = \frac{1}{T} \int_0^T V_s(t) dt = \frac{1}{T} \int_{t_1}^{t_2} V_s(t) dt$$



$$\begin{aligned} V_d &= E \sin(\omega t) \\ \Rightarrow t_1 &= \frac{1}{\omega} \arcsin\left(\frac{V_d}{E}\right) \\ t_2 &= \frac{T}{2} - t_1 \end{aligned}$$

$$V_s = \begin{cases} 0 & \text{si } 0 \leq t \leq t_1 \text{ and } t_2 \leq t \leq T \\ aV_e + b & \text{si } t_1 \leq t \leq t_2 \end{cases}$$

$$a = \frac{R_L}{R_L + R_d}, \quad b = -\frac{R_L}{R_L + R_d} \cdot V_d$$

$$\begin{aligned} \Rightarrow V_s(moy) &= \frac{1}{T} \int_{t_1}^{t_2} (a \cdot E \sin(\omega t) + b) dt \\ &= \frac{aE}{T\omega} \left[-\cos(\omega t) \right]_{t_1}^{t_2} + \frac{b}{T} (t_2 - t_1) \end{aligned}$$

$$V_s(\text{moy}) = \frac{aE}{T \cdot 2\pi} \left[-\cos(\omega t_2) + \cos(\omega t_1) \right] + \frac{b}{T} (t_2 - t_1)$$

$$\Rightarrow V_s(\text{moy}) = \frac{aE}{2\pi} \left[-\cos(\omega t_2) + \cos(\omega t_1) \right] + \frac{b}{T} (t_2 - t_1)$$

avec: $t_1 = \frac{1}{\omega} \arcsin\left(\frac{V_d}{E}\right)$

$$t_2 = \frac{T}{2} - t_1$$

$r_d = 0$ & $V_d = 0$: في حالة ديود مثالي

$$t_1 = 0 \text{ et } t_2 = T/2$$

$$a = 1 \text{ et } b = 0$$

$$V_s(\text{moy}) = \frac{E}{2\pi} \left[-\cos\left(\frac{2\pi}{T} \cdot \frac{T}{2}\right) + \cos(0) \right] + 0$$

$$V_s(\text{moy}) = \frac{E}{\pi} \rightarrow \text{Diode idéale}$$

b) Valeur efficace القيمة الفعالة

$$V_s^2(\text{eff}) = \frac{1}{T} \int_{t_1}^{t_2} V_s^2(t) dt$$

$$V_s(t) = aV_e + b \Rightarrow V_s^2(t) = a^2V_e^2 + b^2 + 2abV_e$$

$$V_s^2(\text{eff}) = \frac{1}{T} \int_{t_1}^{t_2} a^2 V_e^2 dt + \frac{1}{T} \int_{t_1}^{t_2} b^2 dt + \frac{1}{T} \int_{t_1}^{t_2} 2abV_e dt$$

$A_1 \quad A_2 \quad A_3$

$$A_1 = \frac{a^2 E^2}{T} \int_{t_1}^{t_2} \sin^2(\omega t) dt$$

$$= \frac{a^2 E^2}{2T} \int_{t_1}^{t_2} (1 - \cos(2\omega t)) dt$$

$$A_1 = \frac{a^2 E^2}{2T} \left[(t_2 - t_1) - \frac{1}{2\omega} (\sin(2\omega t_2) - \sin(2\omega t_1)) \right]$$

$$A_2 = \frac{b^2}{T} (t_2 - t_1)$$

$$A_3 = 2ab \cdot V_e(\text{moy})$$

$$A_3 = 2ab \cdot \left\{ \frac{aE}{2\pi} \left[-\cos(\omega t_2) + \cos(\omega t_1) \right] + \frac{b}{T} (t_2 - t_1) \right\}$$

$r_d = 0$ et $V_d = 0$: في حالة ديود مثالي

$$a = 1, b = 0$$



$$t_1 = 0, t_2 = T/2$$

$$A_2 = 0, A_3 = 0$$

$$V_s^2(\text{eff}) = \frac{E^2}{2T} \left(\frac{T}{2} \right) = \frac{E^2}{4}$$

$$\Rightarrow V_s(\text{eff}) = \frac{E}{2} \rightarrow \text{Diode idéale}$$

2) Redressement double alternance =

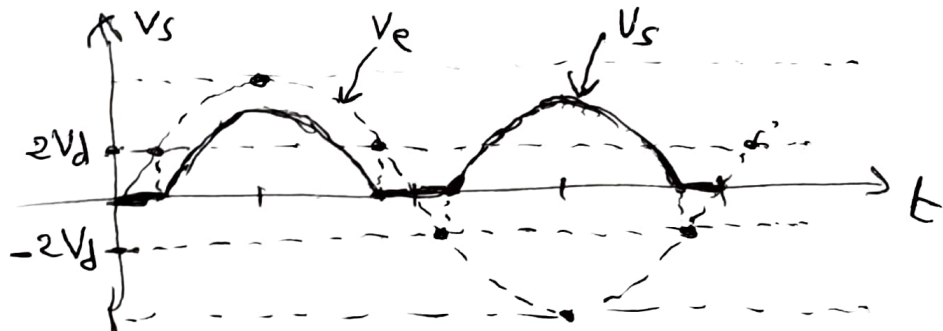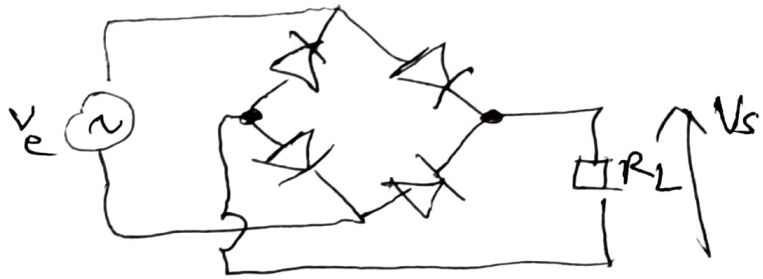

يمكن بدون إعادة الحساب أن نحسب

القيمة المتوسطة والفعالة كما يلي =

$$V_{s(\text{moy})}(\text{Double alternance}) = 2 V_{s(\text{moy})}(\text{simple alternance})$$

$$V_{s(\text{eff})}^2(\text{Double alternance}) = 2 V_{s(\text{eff})}^2(\text{simple alternance})$$

لأن من حالة ديود متناحية =

$$V_{s(\text{moy})} = 2 \frac{E}{\pi}$$

$$V_{s(\text{eff})}^2 = 2 \cdot \frac{E^2}{4} = \frac{E^2}{2}$$

$$\Rightarrow V_{s(\text{eff})} = \frac{E}{\sqrt{2}}$$

