
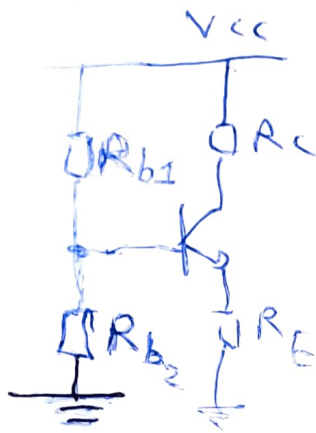


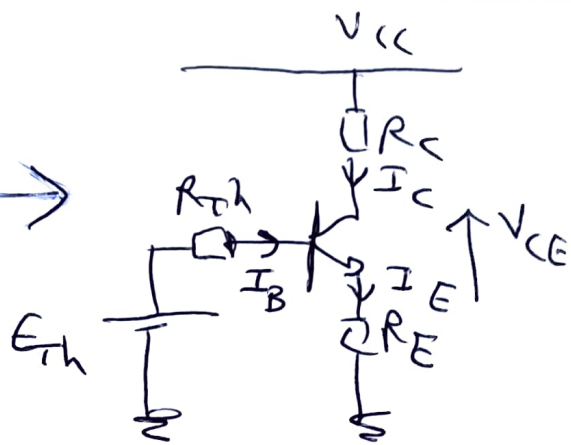D) Droite de charge statique et $Q(V_{CEQ}, I_{CQ}) =$



0.25



$$V_{CC} - R_C I_C - R_E I_E - V_{CE} = 0$$

$$I_E = \left(1 + \frac{1}{\beta}\right) I_C$$

$$\Rightarrow I_C = \frac{-V_{CE} + V_{CC}}{R_C + \left(1 + \frac{1}{\beta}\right) R_E}$$

avec :

$$\begin{cases} I_{Cmax} = \frac{V_{CC}}{R_C + \left(1 + \frac{1}{\beta}\right) R_E} \\ V_{CEmax} = V_{CC} \end{cases}$$

0.25

$$E_{Th} - R_{Th} I_B - V_{BE} - R_E I_E = 0$$

$$\Rightarrow I_{BQ} = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}$$

$$\Rightarrow I_{CQ} = \beta \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}$$

$$\Rightarrow V_{CEQ} = V_{CC} - \left(R_C + \left(1 + \frac{1}{\beta}\right) R_E\right) I_{CQ}$$

0.25

0.25


A.N. =

$$R_{Th} = 8,89 \text{ k}\Omega$$


$$E_{Th} = 1,11 \text{ V}$$

$$I_{Cmax} = 1,9 \text{ mA}, V_{CEmax} = 10 \text{ V}$$
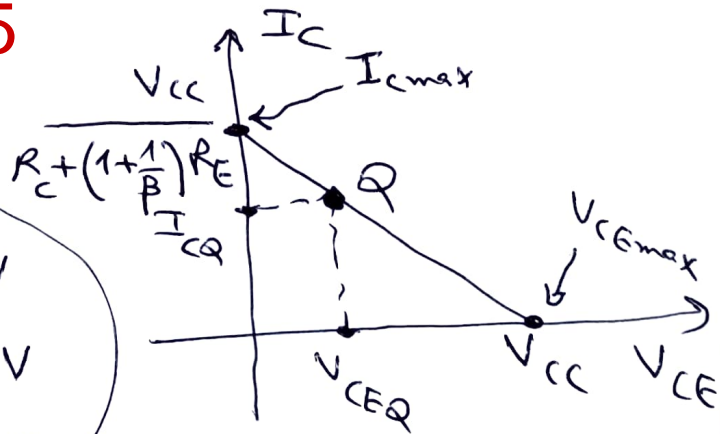
$$I_{CQ} = 1,7 \text{ mA}, V_{CEQ} = 1,28 \text{ V}$$



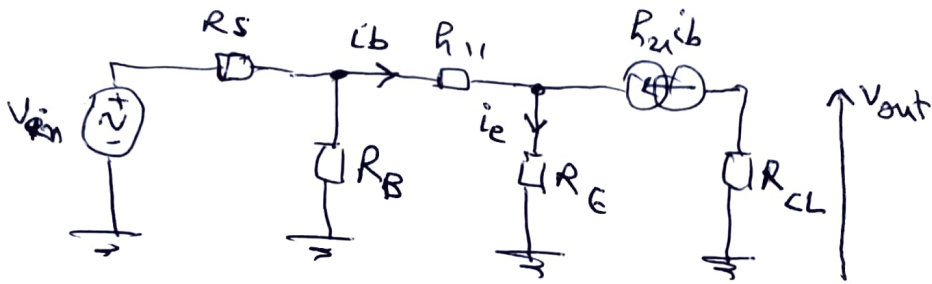2) Schéma équivalent petits signaux (AC) :




01.00

$$R_B = R_{B1} \parallel R_{B2} \quad , \quad R_{CL} = R_C \parallel R_L$$

3) Gain en tension :

$$V_{Th} = \frac{R_B}{R_B + R_S} \cdot V_{in}$$

$$R_{Th} = R_S \parallel R_B$$

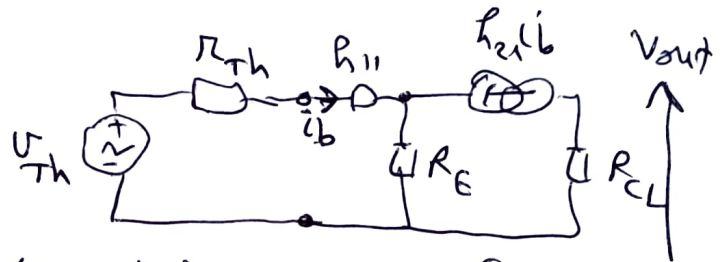

$$V_{Th} - (R_{Th} + h_{11})i_b - R_E(h_{21} + 1)i_b = 0 \quad \text{--- (1)}$$

$$V_{out} = -h_{21}i_b \cdot R_{CL} \quad \text{--- (2)}$$

$$(1) \Rightarrow i_b = \frac{V_{Th}}{R_{Th} + h_{11} + (h_{21} + 1)R_E} \quad \text{--- (3)}$$

$$(3) \rightarrow (2) : V_{out} = -R_{CL} \cdot h_{21} \cdot \frac{V_{Th}}{R_{Th} + h_{11} + (h_{21} + 1)R_E}$$

$$\Rightarrow V_{out} = -h_{21}R_{CL} \cdot \frac{\frac{R_B}{R_B + R_S} \cdot V_{in}}{R_{Th} + h_{11} + (h_{21} + 1)R_E}$$

$$\Rightarrow G_V = \frac{V_{out}}{V_{in}} = -h_{21} \cdot \frac{\frac{R_B R_{CL}}{R_B + R_S}}{R_{Th} + h_{11} + (h_{21} + 1)R_E}$$


$$G_V \approx -h_{21} \cdot \frac{R_{CL}}{h_{11} + h_{21}R_E}$$

A.N. : $G_V = -4,3$

0.25

0.25

④ Résistance d'entrée =

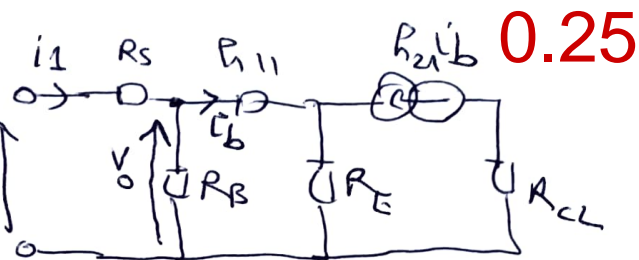

$$V_o = h_{11}i_b + (h_{21}+1)R_E i_b$$

$$\Rightarrow V_o = [h_{11} + (h_{21}+1)R_E] i_b$$

$$V_1 = R_S i_1 + R_B (i_1 - i_b) \quad \text{--- (1)}$$

$$V_o = V_1 - R_S i_1 \quad \text{--- (2)}$$

$$\text{(2)} \Rightarrow i_b = \frac{(R_S + R_B) i_1 - V_1}{R_B} \quad \text{--- (3)}$$

$$\text{(3) \& (4)} \rightarrow \text{(1)} = V_1 - R_S i_1 = [h_{11} + (h_{21}+1)R_E] \cdot \frac{(R_S + R_B) i_1 - V_1}{R_B}$$

$$\Rightarrow V_1 \left[1 + \frac{h_{11} + (h_{21}+1)R_E}{R_B} \right] = \left[R_S + (h_{21}+1) \frac{R_E}{R_B} (R_S + R_B) \right] i_1$$

$$\neq R_e = \frac{V_1}{i_1} = \frac{R_S + (h_{11} + (h_{21}+1)R_E) \left(1 + \frac{R_S}{R_B} \right)}{1 + \frac{h_{11} + (h_{21}+1)R_E}{R_B}}$$

$$= \frac{R_S \left[1 + \frac{h_{11} + (h_{21}+1)R_E}{R_B} \right] + h_{11} + (h_{21}+1)R_E}{1 + \frac{h_{11} + (h_{21}+1)R_E}{R_B}}$$

$$\Rightarrow R_e = R_S + \frac{1}{\frac{1}{R_B} + \frac{1}{h_{11} + (h_{21}+1)R_E}} \quad \text{--- (4)}$$




A.N. := $R_e = 7,83 \text{ k}\Omega$ --- (5)

⑤ Résistance de sortie =



$$R_{eq} = ((R_S // R_B) + h_{11})$$

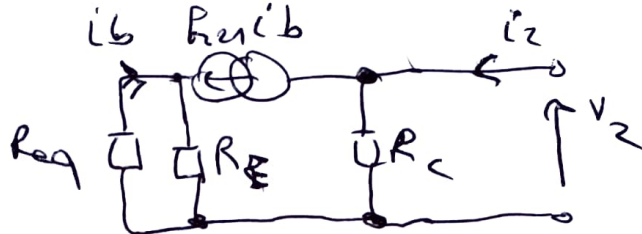

$$V_2 = R_C (i_2 - h_{21} i_b) \quad \text{--- (1)}$$

$$i_b = -\frac{R_E}{R_E + R_{eq}} \cdot h_{21} i_b \Rightarrow i_b = 0 \quad \text{--- (2)}$$


② → ① : $V_2 = R_C i_c \Rightarrow R_{\text{sortie}} = \frac{V_2}{i_2} = R_C$

A.N: $R_{\text{sortie}} = 5 \text{ k}\Omega$

⑥ Tracés de V_{in} et V_{out} :

$$V_{in} = 0,18 \sin(2\pi \cdot 10^4 t) \Rightarrow V_{out} = G_V \cdot V_{in}$$
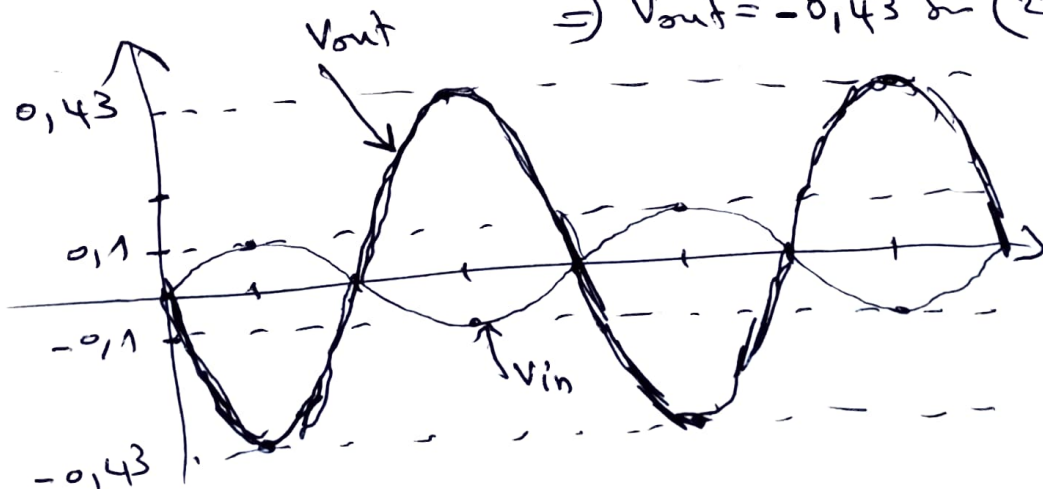
$$\Rightarrow V_{out} = -0,43 \sin(2\pi \cdot 10^4 t)$$



④