



### Homework

على الطالب بذل مجهوده الشخصي في انجاز هذا العمل و ارجاعه قبل 12 ديسمبر 2024.

#### Exercice

Linearize :

$$B(\theta) = \sin^3(\theta)$$

#### Exercice 2

Demonstrate that the effective value of the voltage  $u(t)$  which has the following instantaneous value  $u(t) = U_{max} \sin(\omega t)$  is:

$$U_{eff} = \frac{U_{max}}{\sqrt{2}}$$

#### Exercice 3


The circuit in Figure 1 is supplied by a sinusoidal voltage source expressed in the domain time as:

$$v(t) = 40 \sin(3000t)$$

$$R_1 = 1.5 \text{ } K\Omega \quad C = \frac{1}{6} \mu F \quad L = \frac{1}{3} \text{ H}$$

$$R_2 = 1 \text{ K}\Omega$$

Figure 1

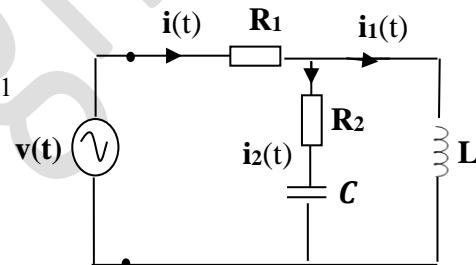

- 1) Calculate the equivalent impedance of this circuit? what is the nature of this impedance?
- 2) Determine The effective value of current I ? deduce the instantaneous value of the current  $i(t)$ ?
- 3) Is the current  $i(t)$  lagging behind the voltage, in phase or leading the voltage  $v(t)$ ? (Justify your answer)
- 4) Determine The effective value of current  $I_1$ ? deduce the instantaneous value of the current  $i_1(t)$  ?
- 5) Determine The effective value of the current  $I_2$ ? deduce the instantaneous value of the current  $i_2(t)$ ?
- 6) Evaluate the power factor?
- 7) Determine the active and reactive power consumed by this impedance?

Good luck