

University of Biskra 2024-2025



Building Physics

LEVEL: 1 YEAR BACHELOR

SPECIALTY: COP

COURS 06

ELECTRICITY



University of Biskra

2024-2025


Ohm's law :

$U = R \cdot I$ is an equation that relates voltage (U), resistance (R), and current (I).

Kirchhoff's laws :


Kirchhoff's laws refer to two fundamental laws in electrical circuit analysis:

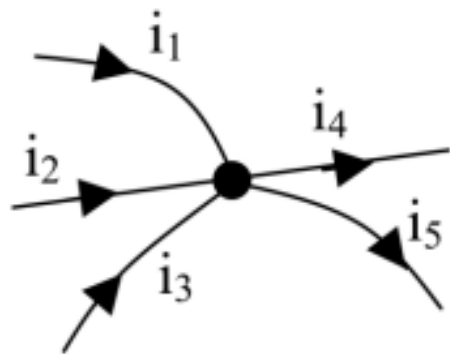Kirchhoff's current law (KCL) states that the total current entering a **junction** in an electrical circuit **must be equal** to the total current **leaving the junction**.



$$\sum_{k=1}^n i_k = 0$$

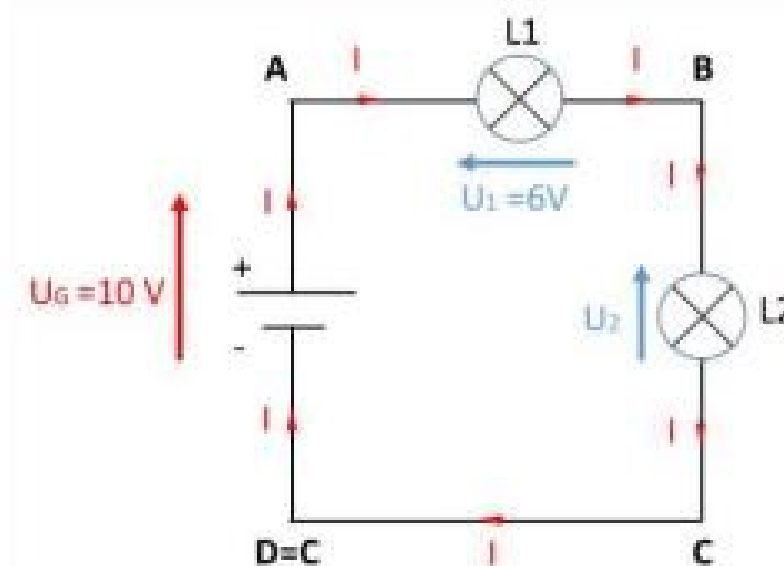Kirchhoff's voltage law (KVL) states that the total voltage around any **closed loop** in an electrical circuit **must be zero**.




$$U_G - U_{L1} - U_{L2} = 0$$

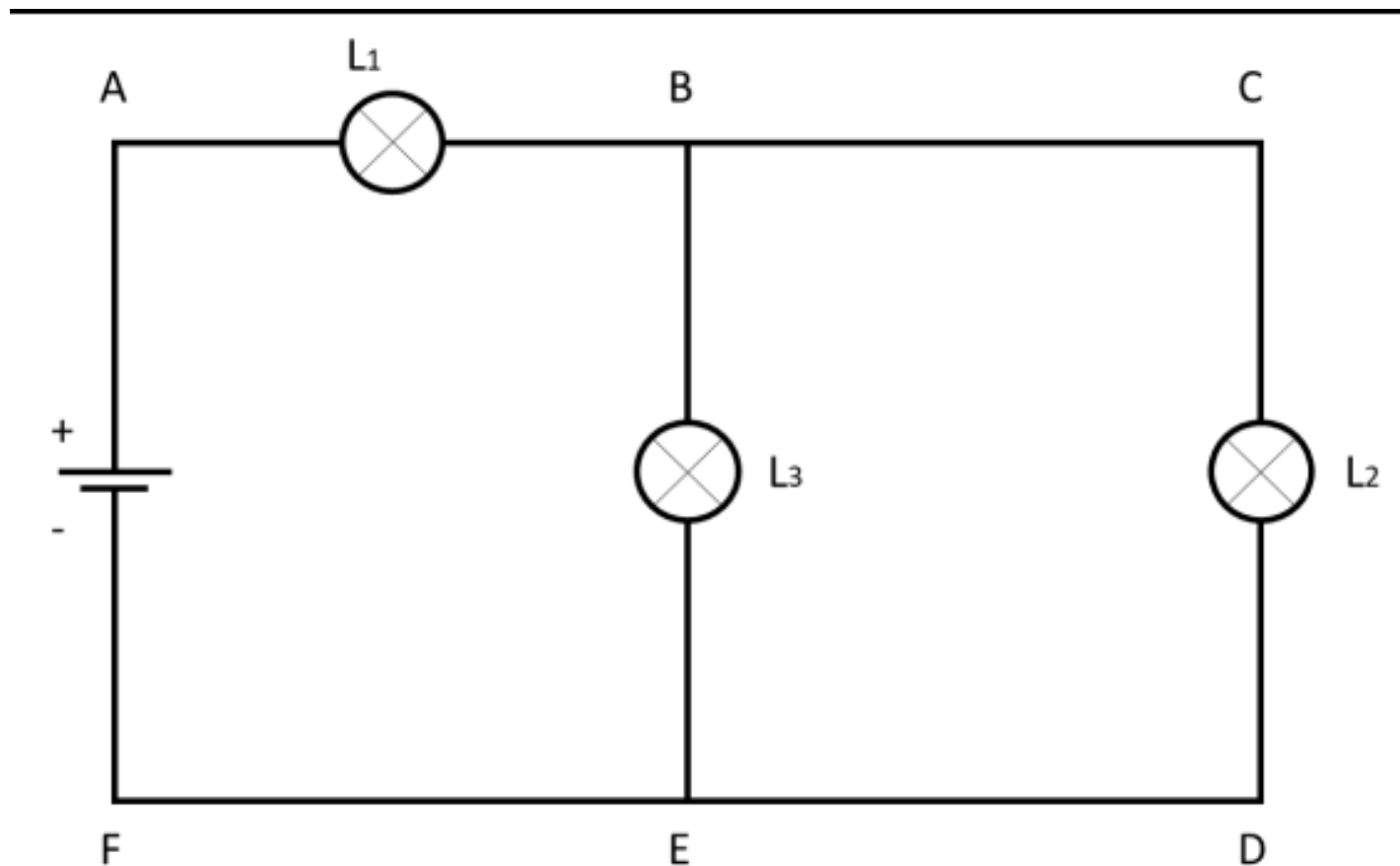Exercise n°1:

Given that the voltage across lamp L1 is equal to 4V and $U_G = 10V$.

Calculate the voltages across lamps L2 and L3.



Solution :

Exercise n°1:

We apply the conservation of potential (the second Kirchhoff law KVL) to the circuit loop **ABCDEF**.

For the first loop **ABEF**:

the first **Kirchhoff law** implies that:

$$U_G - U_{L1} - U_{L3} = 0$$

$$\text{So: } U_{L3} = 10 - 4 = 6V$$

For the second loop BCDE:




The first Kirchhoff law implies that:

$$U_{L3} - U_{L2} = 0$$

This implies that:

$$U_{L3} = U_{L2}$$

$$\text{So: } U_{L2} = 6V$$

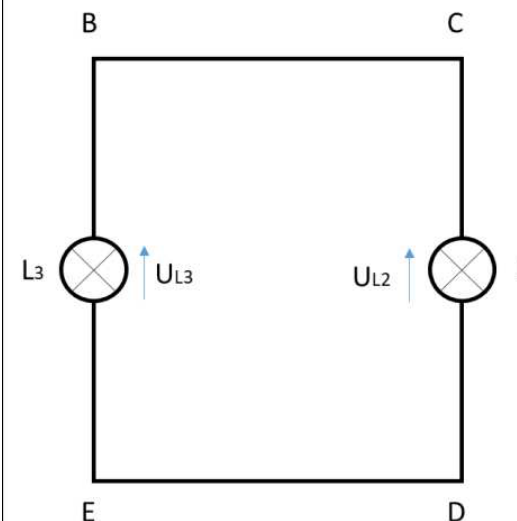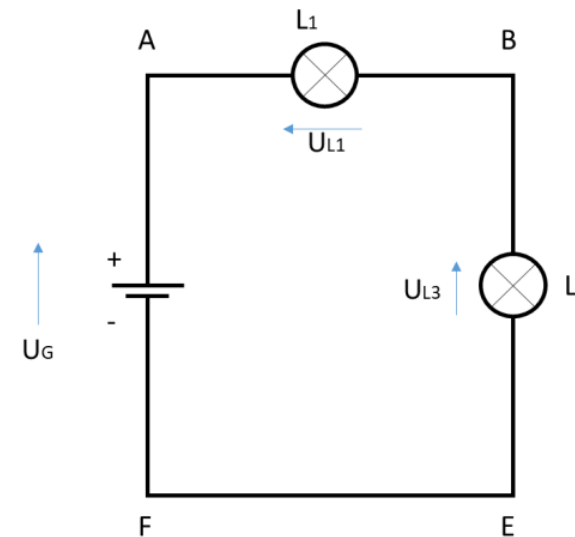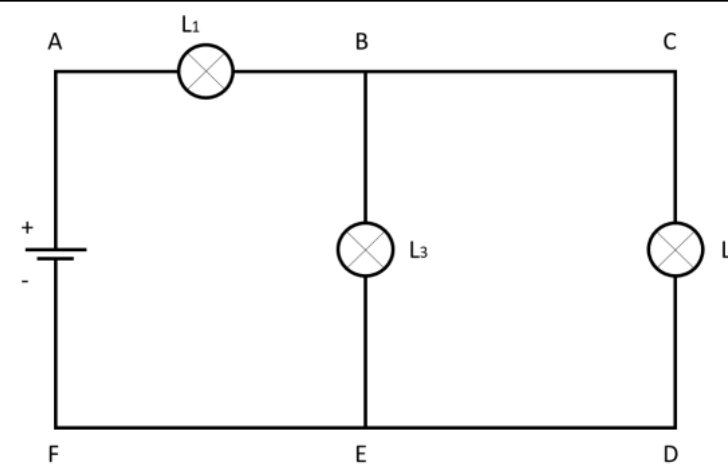


Exercise n°2:

we have the following circuit:

- From F to A, we have a battery P_1 of 10 V, with an internal resistance of $0.5\ \Omega$, in the direction of current i_1 .
- From A to B, there is a resistance R_1 of $2.5\ \Omega$ through which current i_1 flows.
- From B to C, there is a battery P_2 causing a voltage drop of 1 V, with an internal resistance of $0.5\ \Omega$, in the direction of current i_2 .
- From C to D, there is a resistance R_2 of $1.5\ \Omega$.
- From B to E, there is a battery P_3 of 3 V with an internal resistance of $0.5\ \Omega$.
Additionally, there is a resistance R_3 of $1.5\ \Omega$ through which current i_3 flows.

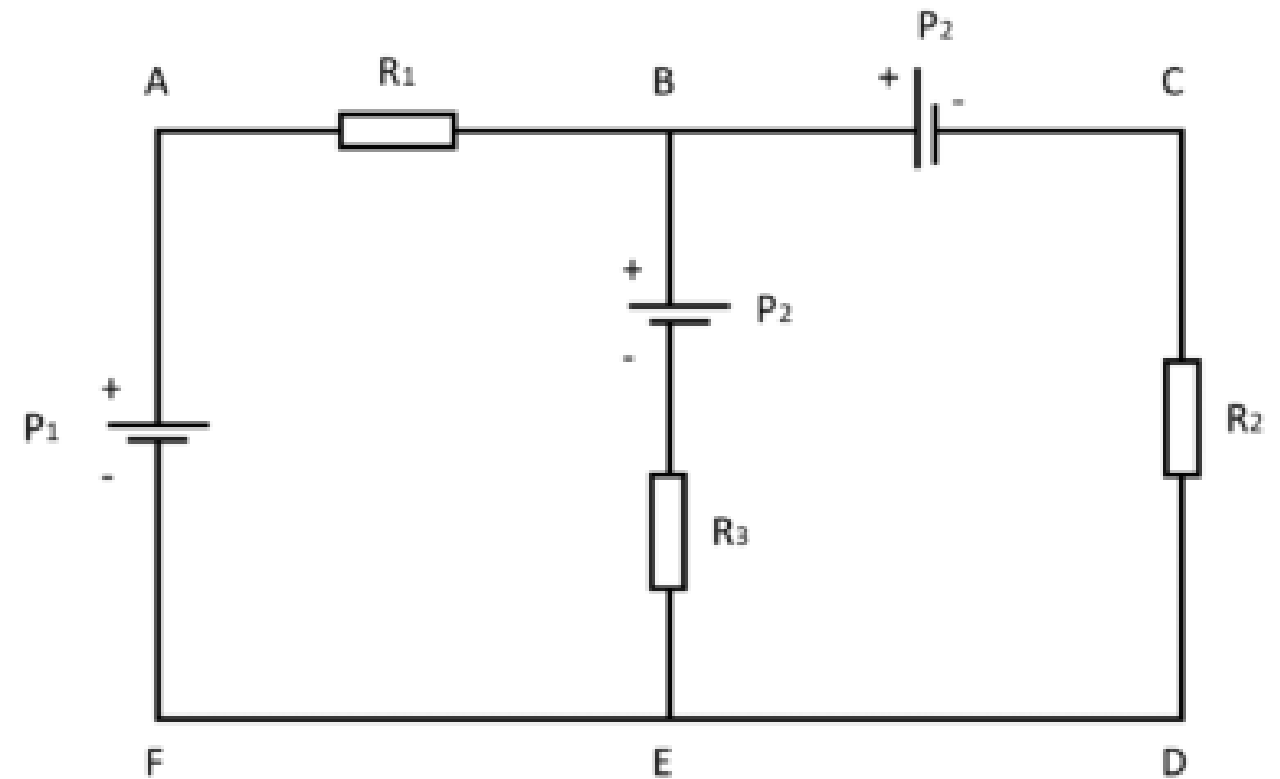Find the values of the two currents i_1 and i_2 , knowing that the current intensity i_3 is equal to 0.5 A.



Solution :

Exercise n°2:

According to the first Kirchhoff law (node law), we have: $\sum I_s = \sum I_e$ Where:


- I_s : currents leaving the node in amperes (A)
- I_e : currents entering the node in amperes (A)

This law implies: $i_1 = i_2 + i_3$

According to **Ohm's law**, we also have: $U = R \cdot I$ Where:

- U : voltage or potential in volts (V)
- R : resistance in ohms (Ω)
- I : current intensity in amperes (A)

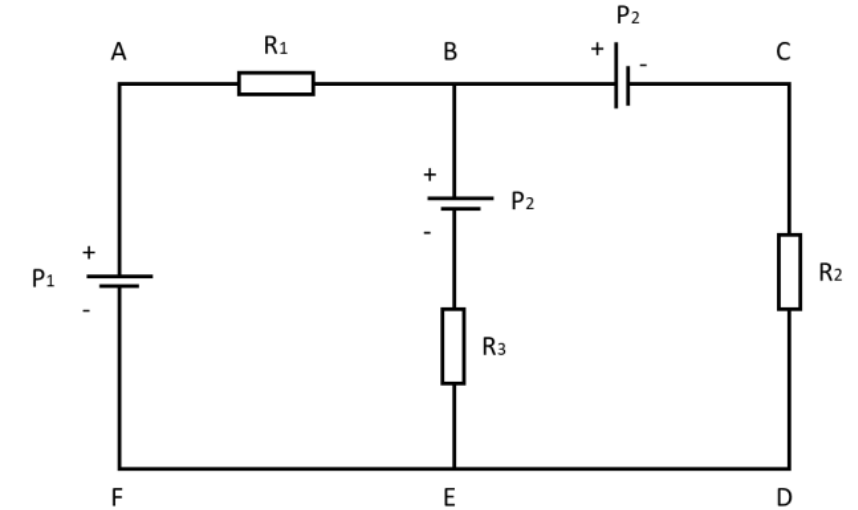Then, we apply the conservation of potential in the circuit **loop ABCDA** according to the second Kirchhoff law (loop law),



In this example, we observe two loops:

ABEFA and **BCDEB**.


From reading the data of the first loop **ABEF**, we have:

$$UG - 0.5i_1 - 2.5i_1 - 0.5i_3 - 3 - 1.5i_3 = 0$$

$$UG - (3i_1) - (2i_3) - 3 = 0$$

Substituting UG with 10V and i_3 with 0.5A, we obtain:
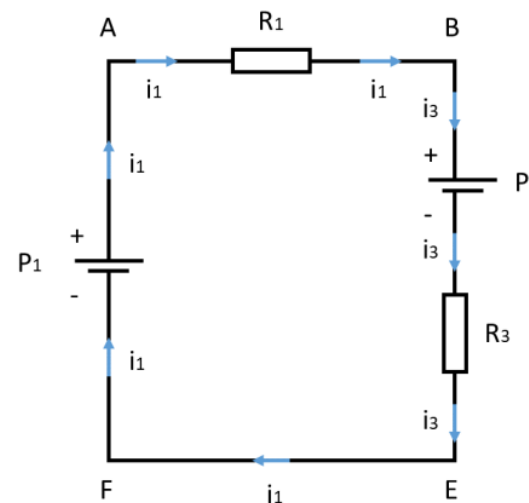
$$-3i_1 = -6 \quad \text{So: } i_1 = 2A$$




From reading the data of the second loop **BCDE**, we can deduce that:

$$1.5i_3 + 3 + 0.5i_3 - 1 - 0.5i_2 - 1.5i_2 = 0$$

$$\text{Thus: } 2i_3 - 2i_2 + 2 = 0$$

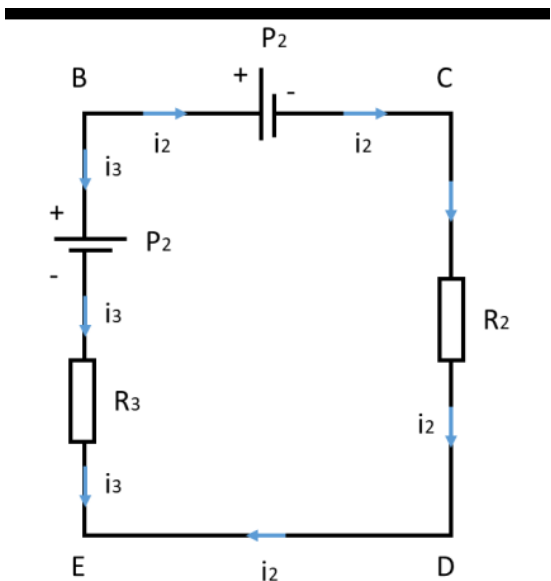Substituting i_3 with 0.5A, we get: **$i_2 = 1.5A$**





Building Physics

LEVEL: 1 YEAR BACHELOR

SPECIALTY: COP



Merci pour

votre Attention

