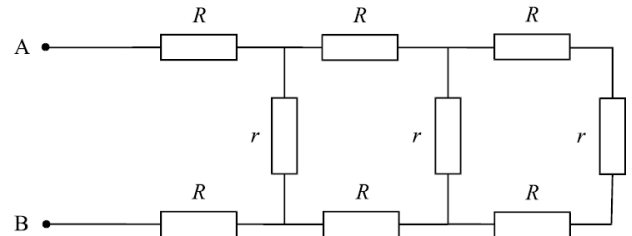


## Fondamental Electricity

### Tutorial N°1 (continuous regime )


#### Exercise 1: Calculation of the equivalent resistance of a network of multiple resistors

- Determine the equivalent resistance  $R_{eq}$  of the dipole AB shown in the following figure.


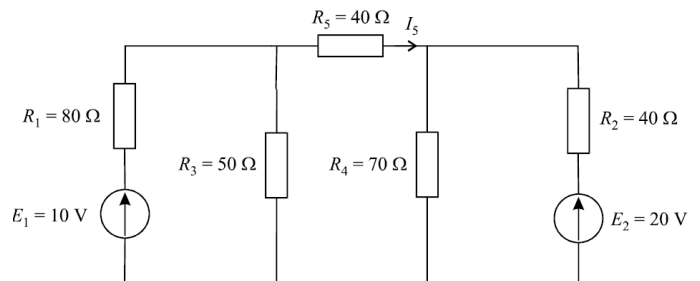
#### Exercise 2: Calculation of a current in a three-mesh circuit powered by two generators


- Determine the current  $I_5$  flowing through resistor  $R_5$  in the circuit shown in the figure.



#### Exercise 3: Application of the voltage divider principle


Consider the circuit shown in the following Figure

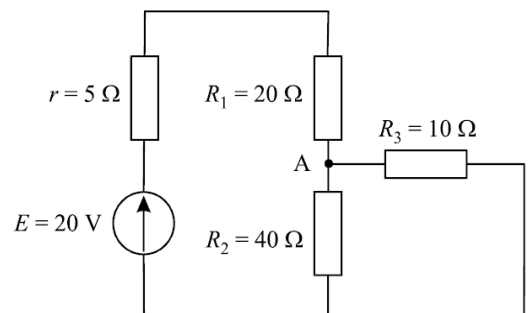1. Determine the potential at point A without using Kirchhoff's laws.
2. Deduce the currents in the different branches of the circuit.
3. Then verify Kirchhoff's node law at point A.



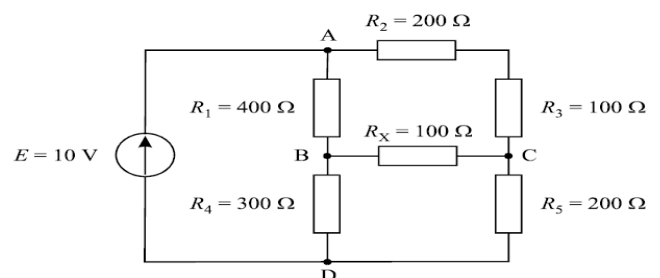
#### Exercise 4: Calculating a current using Millman's theorem

- In the circuit shown in the following figure, determine the value of the current flowing through resistor  $R_X$ .



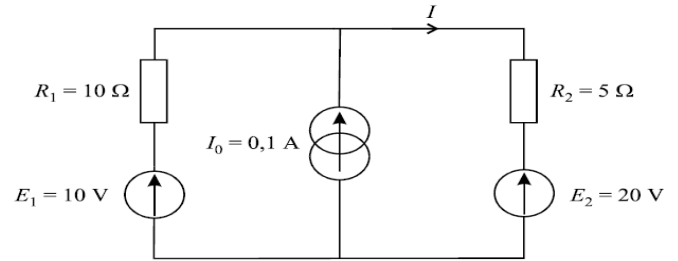
### Exercise 5: Application of the superposition principle in a three-generator circuit

- Dans le montage représenté sur la figure, déterminer le courant  $I$  dans la résistance  $R_2$


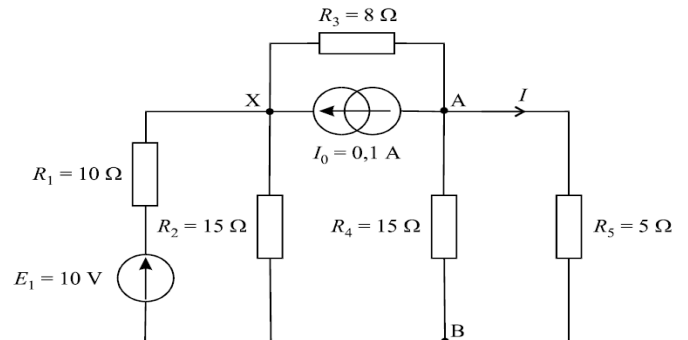
### Exercise 6: Calculation of a current using successive Thévenin Norton transformations

- Determine the current  $I$  in resistor  $R_5$  of the circuit shown in the figure.



### Exercise 7 : Triangle star transformation

Consider the combination of three resistors  $R_1$ ,  $R_2$  and  $R_3$ , shown in a triangle in Figure 1. Let  $I_A$ ,  $I_B$  and  $I_C$  be the currents entering points  $A$ ,  $B$  and  $C$  respectively, and  $V_A$ ,  $V_B$  and  $V_C$  the voltages at these same points.

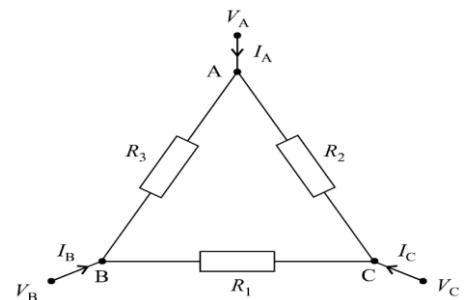


Figure1

We propose to demonstrate that there is a star connection equivalent to this delta connection, in other words, to show that there is a diagram such as the one shown in Figure 2, for which the currents  $I_A$ ,  $I_B$  and  $I_C$  are unchanged, and this for the same values of the voltages at points  $A$ ,  $B$  and  $C$ . We propose to determine the values of  $R_1$ ,  $R_2$  and  $R_3$  as a function of  $R_A$ ,  $R_B$  and  $R_C$ .

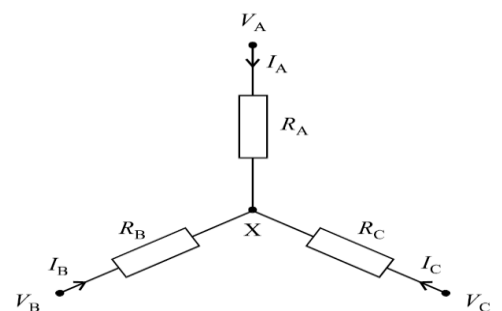


Figure2

- In the circuit shown in Figure 2, apply Millman's theorem to point  $X$  and express  $V_X$  in terms of  $V_A$ ,  $V_B$ , and  $V_C$

- b) Deduce the values of currents  $I_A$ ,  $I_B$ , and  $I_C$  in terms of  $V_A$ ,  $V_B$ , and  $V_C$  on the one hand, and  $R_A$ ,  $R_B$ , and  $R_C$  on the other.
- c) In the circuit shown in Figure 1, determine the currents  $I_A$ ,  $I_B$ , and  $I_C$  as a function of  $V_A$ ,  $V_B$ , and  $V_C$  on the one hand, and  $R_1$ ,  $R_2$  and  $R_3$  on the other.
- d) Deduce the values of  $R_1$ ,  $R_2$  and  $R_3$  as a function of  $R_A$ ,  $R_B$ , and  $R_C$
- e) Consider the circuit shown in Figure 3. Using the previous results and calculating the equivalent resistance of the entire network of resistors, determine the current  $I$  in the circuit.

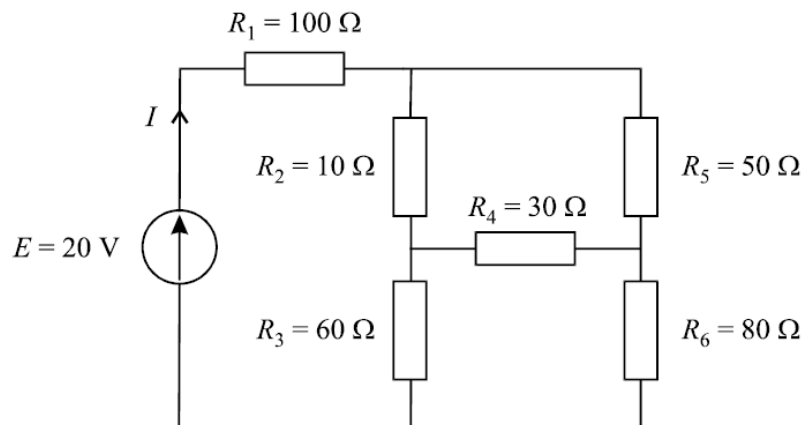


Figure 3

### Exercise 8 : Power consumption in a circuit powered by two DC generators

In the circuit shown in the figure below, determine the average power consumed by each resistor, as well as the power delivered by each of the two generators. Verify the principle of power conservation in this circuit.

