

Exercise n°1

The semi-controlled half-wave rectifier shown in Fig.1; supplies an inductive load $R=8\Omega$, $L=8\text{mH}$. $v_s(t) = -v_s(t) = 220\sqrt{2} \sin(314) t$ $\alpha = \pi + \frac{\pi}{3}$, $\beta = 200^\circ$.

1. State the rule that determines which diode conducts when several diodes share a common cathode.
2. State the rule that determines which diode conducts when several diodes share a common anode.
3. Complete the following table :

TIMES			
D			
T			
u_c			
V_D			
V_T			

4. Plot the waveforms of u_c , i_c , V_T , and V_D , indicating which switches are conducting.
5. Calculate the average value of the load voltage u_c .

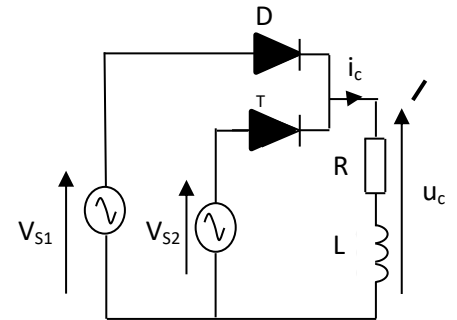


Figure1

Exercise n°2

The controlled single-phase bridge rectifier shown in Figure 2 supplies a highly inductive load ($R-L$; $L \gg R$) with a constant current of 60 A. $V_s=120\text{V}/50\text{Hz}$ et $\alpha = \pi/3$.

- 1) Plot the waveforms of u_c , i_c , i_s , and V_{Th1} .
- 2) Calculate the average and RMS values of the load voltage u_c .
- 3) Calculate the RMS value of the source current i_s .
- 4) Calculate the power factor $\cos \phi$ of the source.

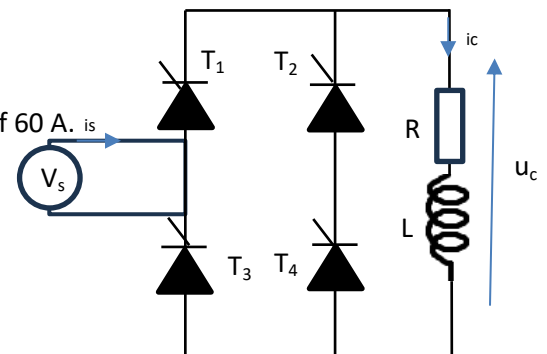


Figure 2

Exercise 03

A single-phase asymmetric mixed bridge connected to the grid 230 V / 50 Hz supplies a DC motor modelled by an RLE load

1. In continuous conduction, with $E = 100 \text{ V}$, $L = 1 \text{ H}$, $R = 0.92 \Omega$, and $\alpha = 60^\circ$, calculate the average voltage of the load (u_{c_avg}), the average current (i_{c_avg}), and the power delivered to the back Back-EMF E .
2. In discontinuous conduction, for $E = 100 \text{ V}$, $L = 0$, $R = 10 \Omega$, and $\alpha = 90^\circ$, plot $u_c(t)$ and $i_c(t)$. Then, for $\alpha = 60^\circ$ and a non-zero inductance L that is insufficient to maintain continuous conduction, draw the waveforms of $u_c(t)$, $i_c(t)$, and $i_s(t)$.

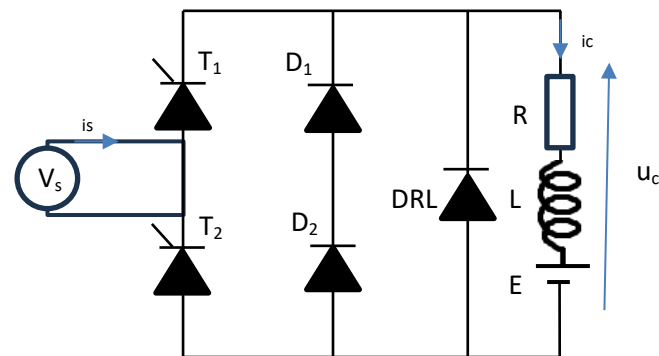


Figure 3