

Ministry of Higher Education and Scientific Research
 University of Biskra
 Faculty of Science and Technology
 Department of Electrical Engineering



Practical work $N^{\circ} - 3$

Supercapacitor modeling

1 Two-branch model

It's a simple electrical circuit model subject to localized constant models, and faithfully describes the electrical behavior of the supercapacitor.

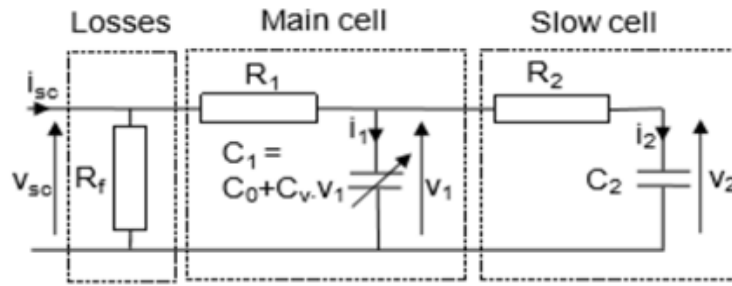


Figure 1: Two-branch model.

$$V_{sc} = V_1 + R_s \cdot i_s \quad (1)$$

With : V_1 : The voltage at the terminal of C_1 in (V).

R_1 : The resistance value of the main branch in (Ω).

The supply current is shown as follows:

$$i_{sc} = i_1 + i_2$$

Or: i_1 : The current at the input of capacitor C_1 in (A).

i_2 : The current at the input of capacitor C_2 in (A).

The capacitance C_1 of capacitor 1 is given by :

$$C_1 = C_0 + C_v \cdot V_1.$$

$$V_1 = \frac{-C_0 + \sqrt{C_0^2 + 2C_v}}{C_v \cdot Q_1}$$

The total terminal voltage of a group of supercapacitors connected in series and in parallel is :

$$U_{sc} = N_s \cdot V_{sc} = N_s \cdot (R_1 \cdot I_{sc} + V_1) \quad (2)$$

We use a DC current source equal to 250 A knowing that :

$$R_1 = 0.00036\Omega, R_2 = 1.92\Omega, C_0 = 2100F, C_v = 623F/V, C_2 = 172F, N_s = 6, N_p = 6,$$

1.1 Equivalent electrical model of a supercapacitor

(Simulation time 200 s)

Demonstrate the model using the expressions in figure-2 ? Realize and visualize all

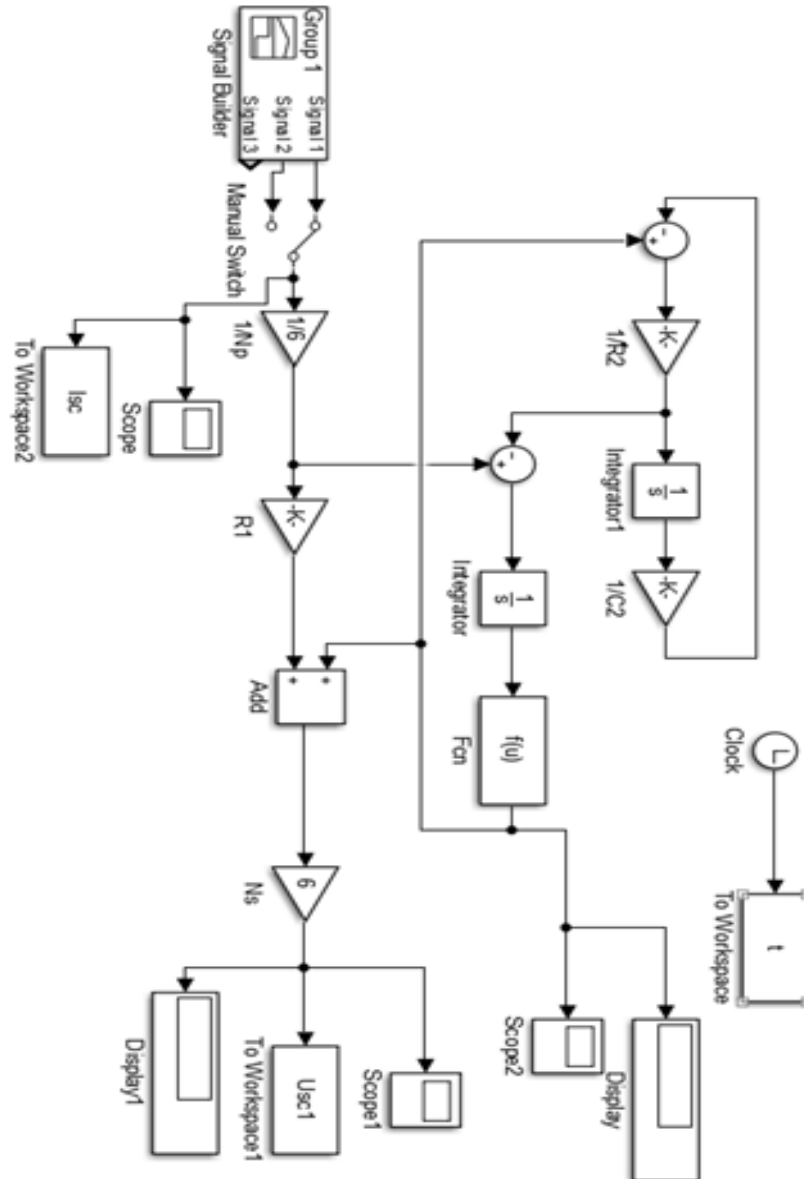


Figure 2: Equivalent electrical model of a supercapacitor in Simulink .

curves.(Simulation time 280000 s).

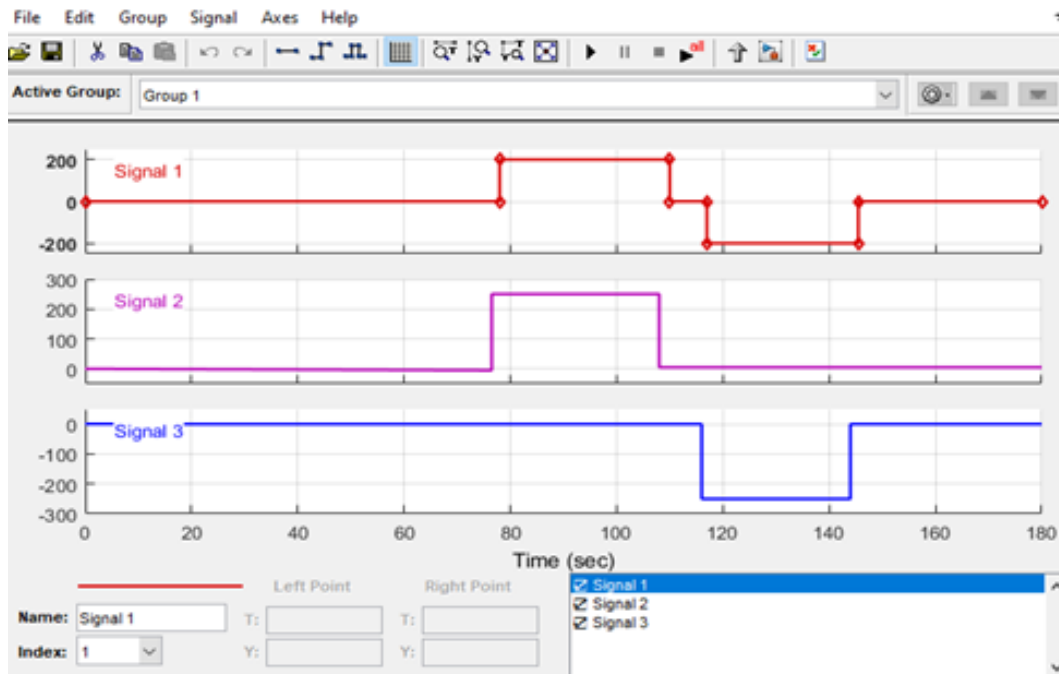


Figure 3: Signal builder curves

1.2 Questions

- ❶ What is the purpose of Practical work ?
- ❷ How does this block work ?
- ❸ What did you visualize with the oscilloscope ?
- ❹ Interpret and conclude the results