




Mohamed Khider University of Biskra
Faculty of Medicine
1st Year Medicine

Academic Year 2025-2026

Series 4
Bioelectricity: Membrane Potential (Nernst Equation)
Equilibrium Donnan

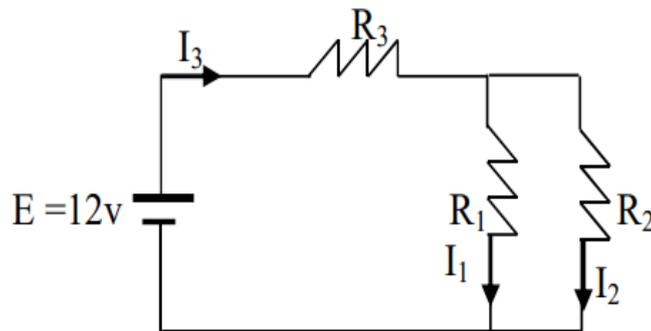Exercise 1 :

Calculate the currents I_1 , I_2 , and I_3 .




Numerical data:

$R_3 = 820 \Omega$, $R_1 = 330 \Omega$ and $R_2 = 220 \Omega$

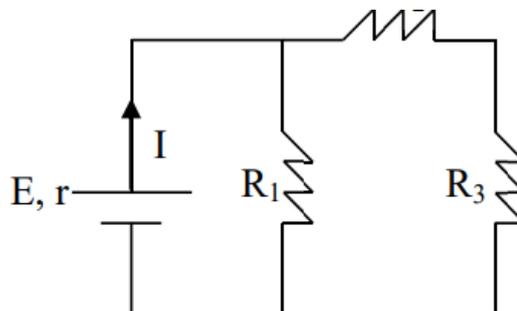Exercise 2:

A battery with electromotive force (emf) $E = 10^5 \text{ V}$ and internal resistance $r = 0.5 \Omega$ supplies the circuit shown opposite.

The resistances R_1 , R_2 , and R_3 have respective values of 20Ω , 5Ω and 15Ω .



Questions

- a- Calculate the equivalent resistance of the entire circuit.
- b- Calculate the current delivered by the battery.
- c- Calculate the potential difference (voltage) across the terminals of the battery.

Exercise 3:

A cell membrane is permeable only to potassium ions K^+ . The temperature is $37^\circ C$. Potassium concentrations are:

- Inside the cell: $[K^+]_{in} = 140 \text{ mM}$
- Outside the cell: $[K^+]_{out} = 5 \text{ mM}$

Questions

- a- Calculate the equilibrium (Nernst) potential for K^+
- b- Interpret the sign of the result.
- c- Explain the physiological meaning of this potential.

Exercise 4:

Two parallel plates with surface area $S = 25 \text{ cm}^2$, separated by 5 cm, are vertically immersed in a solution containing K^+ ions.

A potential difference of 20 V applied across the plates produces an electric current of 0.1 A.

- a- Calculate the concentration of K^+ ions in this solution.

$$\mu_{K^+} = 7.6 \times 10^{-8} \text{ m}^2 \text{ s}^{-1}, F = 96500$$

Exercise 5:

We have a car battery with an electromotive force (EMF) $E = 12 \text{ V}$ and an internal resistance $r = 10 \text{ M}\Omega$.

A copper wire with resistivity $\rho = 1.7 \times 10^{-8} \Omega \cdot \text{m}$, length 50 cm, and cross-sectional area 1 mm^2 is connected across the battery terminals.

Questions

- a- Calculate the resistance R of the wire.
- b- Calculate the current flowing through the wire.
- c- Calculate the thermal power dissipated by the wire.

Exercise 6:


We consider two compartments, A and B, of constant volume, separated by a membrane that is permeable to K^+ and Cl^- ions but impermeable to Y^- ions. The ionic concentrations are as follows:

Compartment A:

$$[K^+]_A = [Y^-]_A = 0.1 \text{ M}$$

Compartment B:

$$[K^+]_B = [Cl^-]_B = 0.1 \text{ M}$$

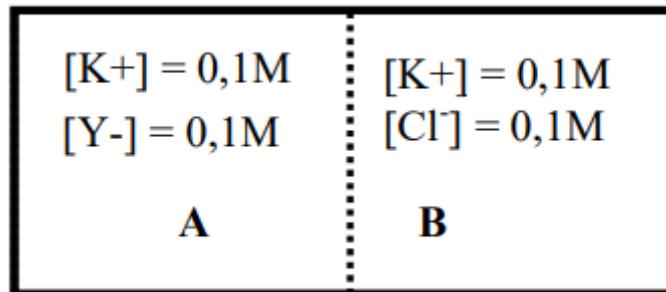

Questions

- In what sense is the membrane separating A and B a Donnan membrane? What does the Gibbs-Donnan equation describe?
- Are the ions at equilibrium?
- At equilibrium, what will be the concentrations of the different ions in each compartment? What will be the potential difference between A and B?

B. BOUDOUR